

ELEC 4700 Assignment 4

By Arjun Bhatti 100915440

Q1 In this part we analyse the circuit , determine G & C matrices. Using nodal analysis to describe the following system of differential equations:

$$V1 = Vin$$

$$G1(V2 - V1) + C1 \frac{d(V2 - V1)}{dt} + Il = 0$$

$$G3V3 - Il = 0$$

$$G3V3 - I3 = 0$$

$$G4(Vo - V4) + GoVo = 0$$

$$V2 - V3 - L \frac{dIl}{dt} = 0$$

$$V4 - aI3 = 0$$

Code : figure 1

```
%%%%%%%%%%%%%%
R1 = 1;
R2 = 2;
C = 0.25;
L = 0.2; %inductance
R3 = 10;
a = 100;
R4 = 0.1;
R0 = 1000;

G1 = 1/R1;%conductance
G2 = 1/R2;
G3 = 1/R3;
G4 = 1/R4;
C_matrix = [0 0 0 0 0 0 0;
            -C C 0 0 0 0 0;
            0 0 -L 0 0 0 0;
            0 0 0 0 0 0 0;
            0 0 0 0 0 0 0;
            0 0 0 0 0 0 0;
            0 0 0 0 0 0 0;];
```


```

G_Matrix = [1 0 0 0 0 0 0;
            -G2 G1+G2 -1 0 0 0 0;
             0 1 0 -1 0 0 0;
             0 0 -1 G3 0 0 0;
             0 0 0 0 -a 1 0;
             0 0 0 G3 -1 0 0;
             0 0 0 0 0 -G4 G4+G1];

F = zeros(7,1);V = zeros(7,1);

count = 1;
for i = -10:10
    F(1) = i;
    V = G_Matrix\F;
    Vdc(count) = V(5);
    V3(count) = V(3);
    count = count + 1;
end
figure(1)
plot(linspace(-10,10,21),Vdc)
hold on
figure(2)
plot(linspace(-10,10,21),V3)
title('Output Voltage Vs Input Voltage')
legend('Vo', 'V3')

```

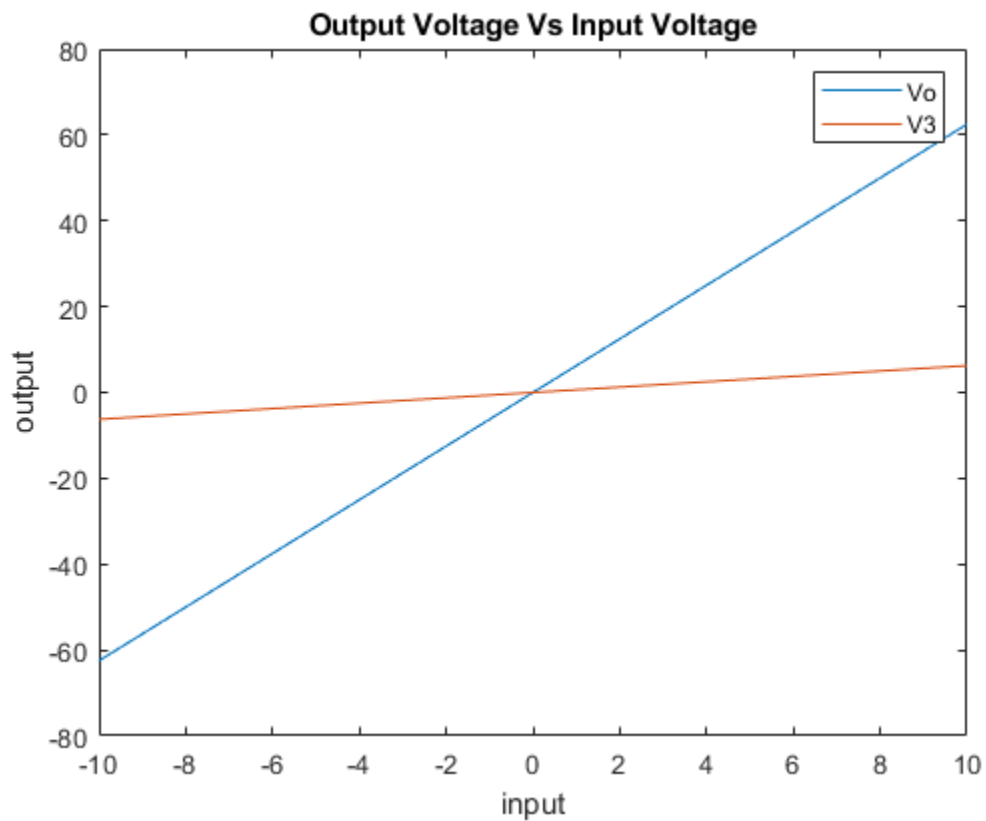

```

%% AC simulations - (jwC + G)V = F(w)

```

```

j = sqrt(-1);
count = 1;
F(1) = 1;
for w = 0:1000
    Gc = G_Matrix + j*w*C_matrix;
    V = Gc\F;
    Vac(count) = V(5);
    count = count+1;
end

figure(2)
plot(0:1000,abs(Vac))
title('Output Voltage vs Frequency')
xlabel('Frequency (rad/s)')

figure(3)
semilogx(0:1000, log10(abs(Vac)))
title('Gain vs Frequency')
xlabel('Frequency (rad/s)')
ylabel('Gain (dB)')

plot(linspace(-10,10,21),V3)
title('Output Voltage Vs Input Voltage')

```

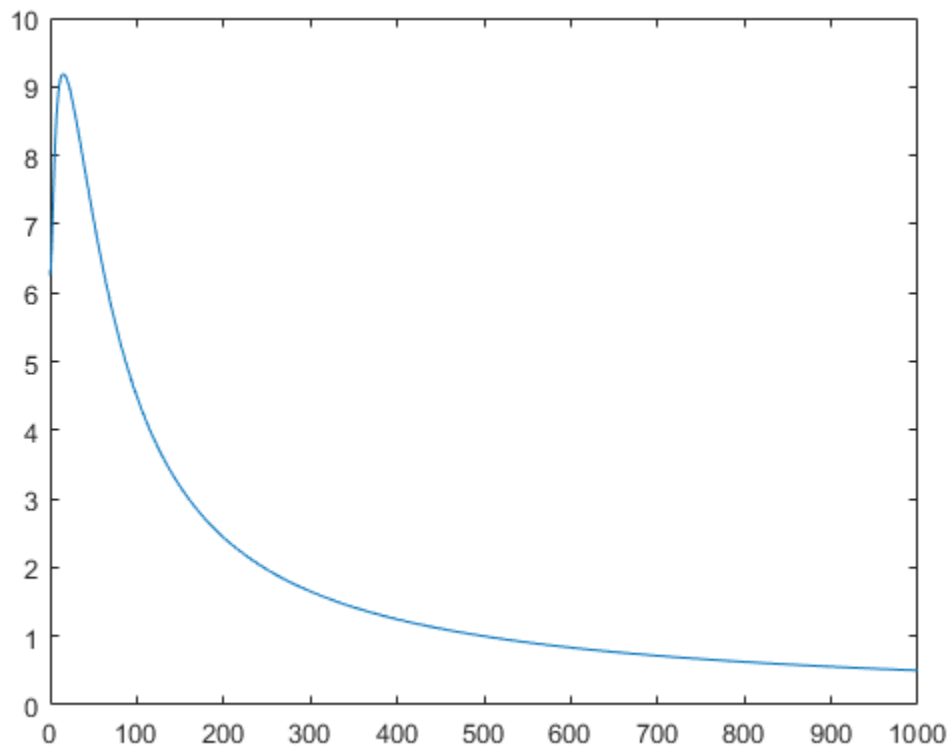


Figure 1 Figure 2

```

plot(linspace(-10,10,21),V3)



```

```

title('Output Voltage Vs Input Voltage')

C_random = C_matrix;
for i = 1:1000
    Cr = normrnd(C,0.05);
    C_random(2,1) = -Cr;
    C_random(2,2) = Cr;
    V = (j*pi*C_random + G_Matrix)\F;
    V_rand(i) = V(5);
end
histogram(abs(V_rand));
title('random perturbations on C using a normal distribution with std = .05')
xlabel('Gain')
ylabel('# of Occurences')

```

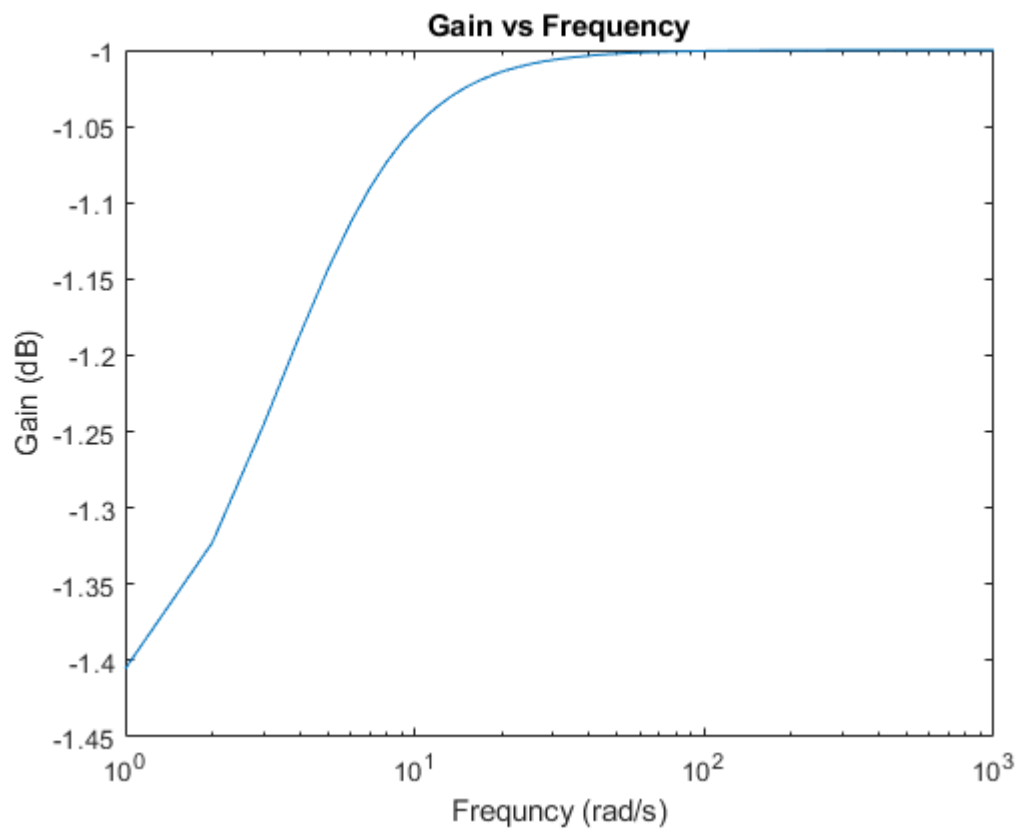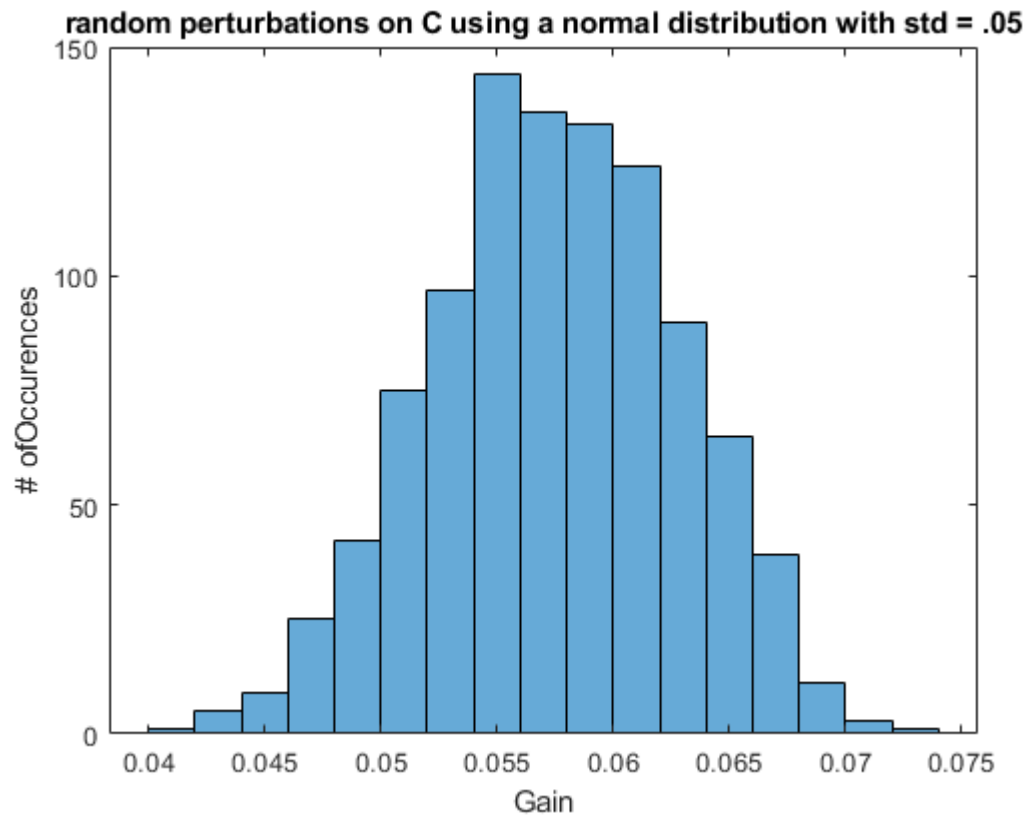

d

Transient

%% transient simulation we must solve $VdV/dt + GV = F$, we must use finite method.Giving us

$\%(C/dt + G)V(j) = CV(j-1)/dt + F(t(j))$

dt = 0.001;

Atrans = C_matrix/dt + G_Matrix;

V1 = zeros(7,1);

V2 = zeros(7,1);

V3 = zeros(7,1);

Vo1(1) = 0;

Vo2(1) = 0;

Vo3(1) = 0;

Vi1(1) = 0;

Vi2(1) = 0;

Vi3(1) = 0;

F1 = zeros(7,1);

F2 = zeros(7,1);

F3 = zeros(7,1);

count = 1;

for t = dt:dt:1

if t >= 0.03

F1(1) = 3;

end

F2(1) = sin(2*pi*t/0.03);

F3(1) = exp(-0.5*((t - 0.06)/0.03)^2);

V1 = Atrans\ (C_matrix*V1/dt + F1);

V2 = Atrans\ (C_matrix*V2/dt + F2);

V3 = Atrans\ (C_matrix*V3/dt + F3);

Vi1(count +1) = V1(1);

Vi2(count +1) = V2(1);

Vi3(count +1) = V3(1);



Vo1(count +1) = V1(5);



Vo2(count +1) = V2(5);



Vo3(count +1) = V3(5);



count = count+1;

end

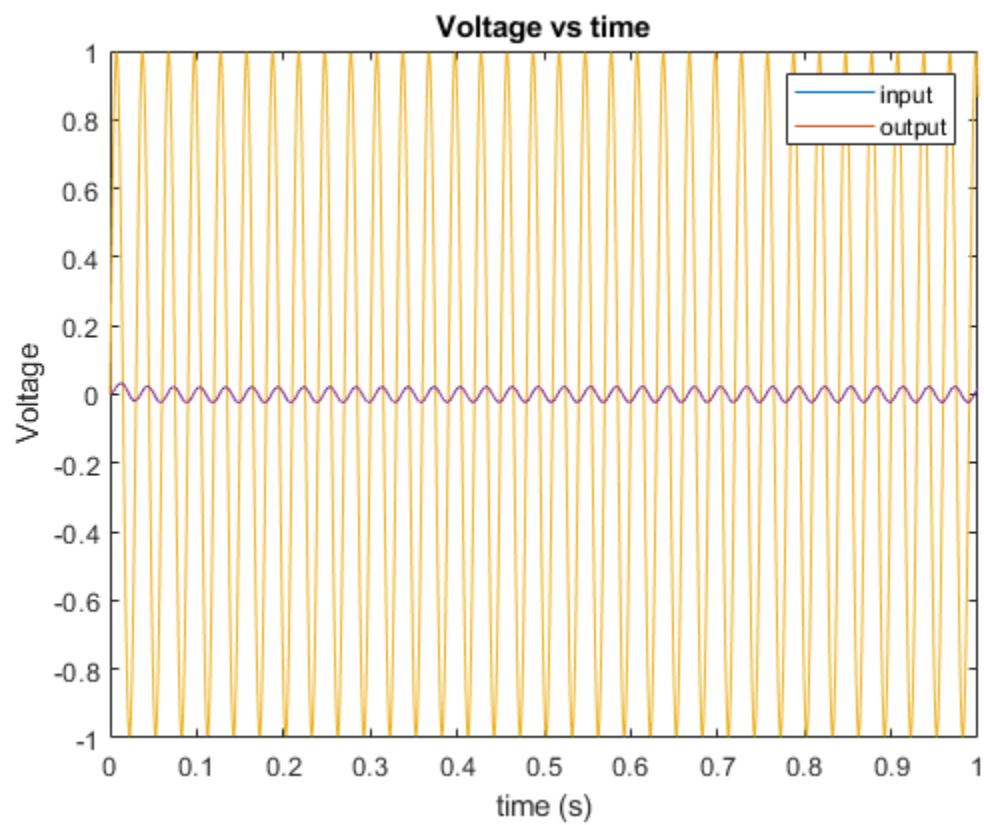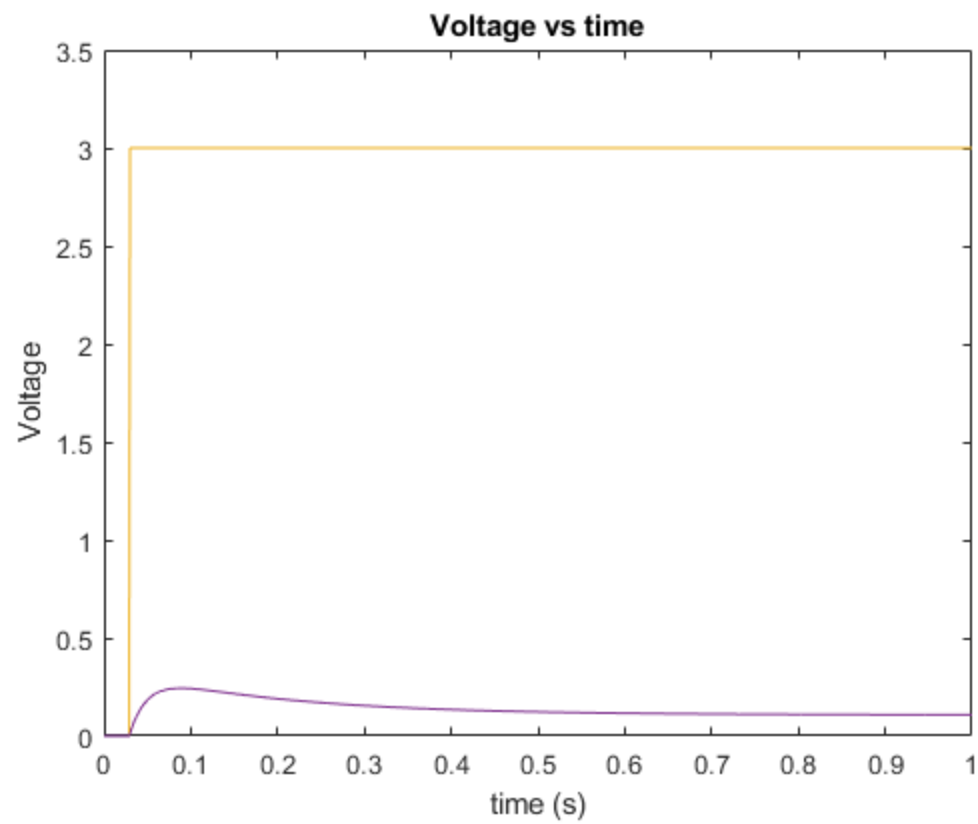

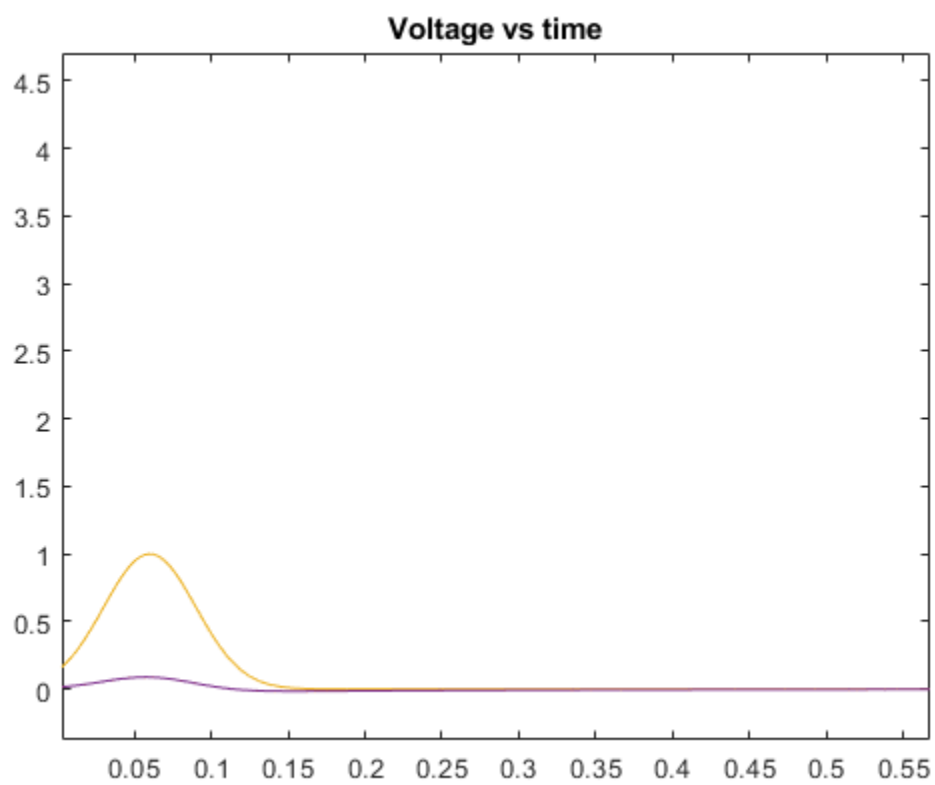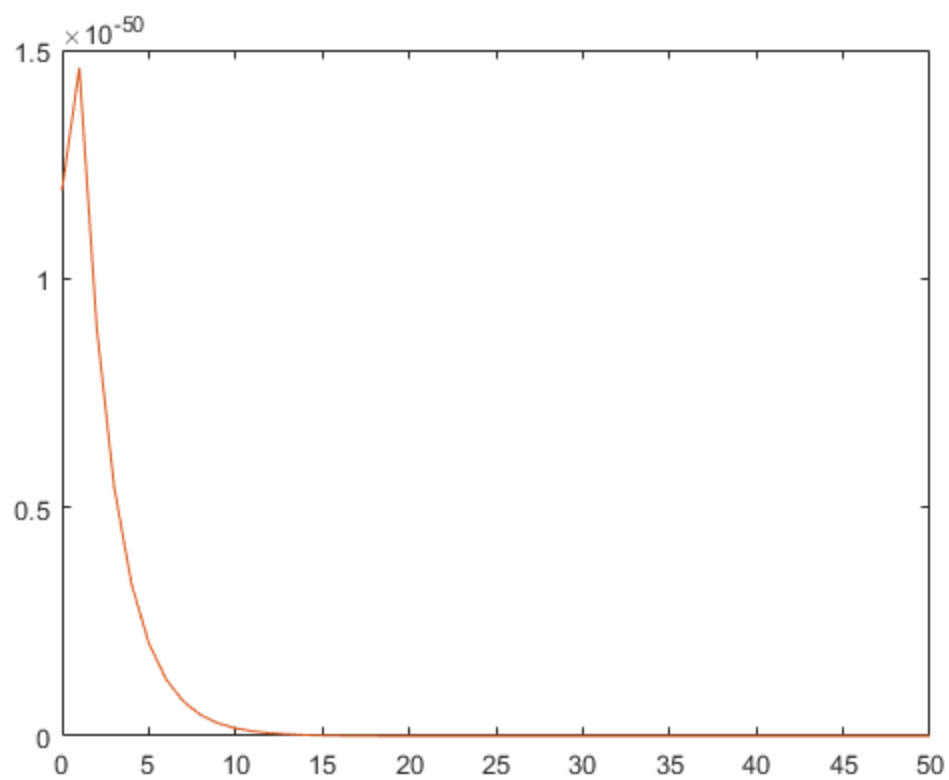

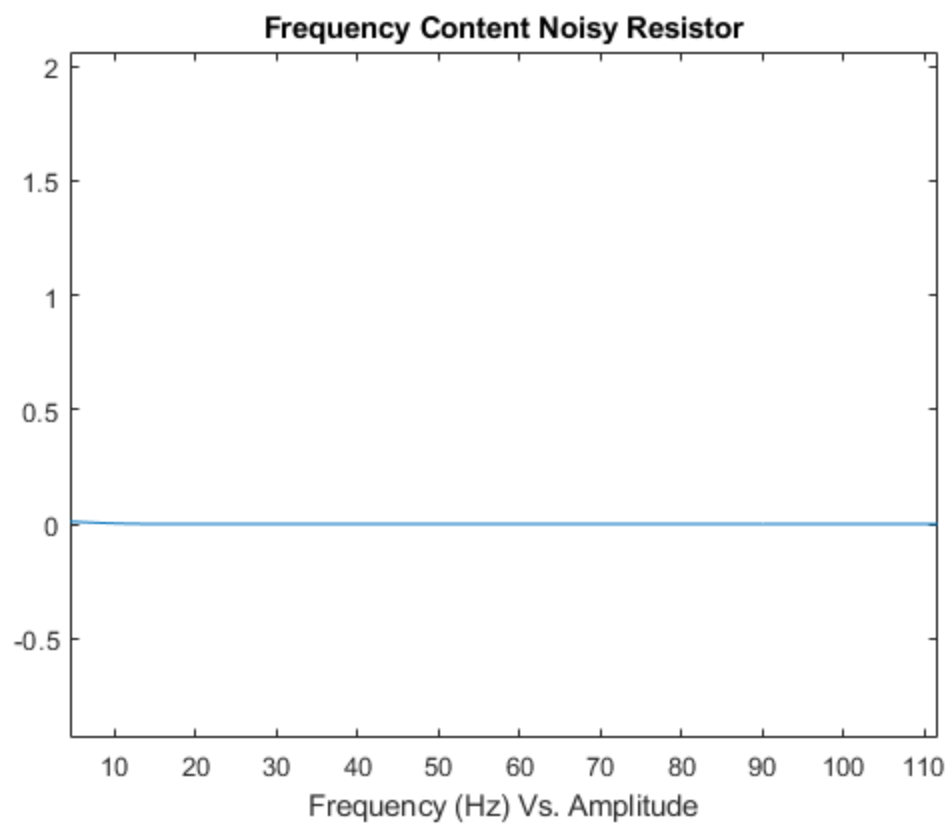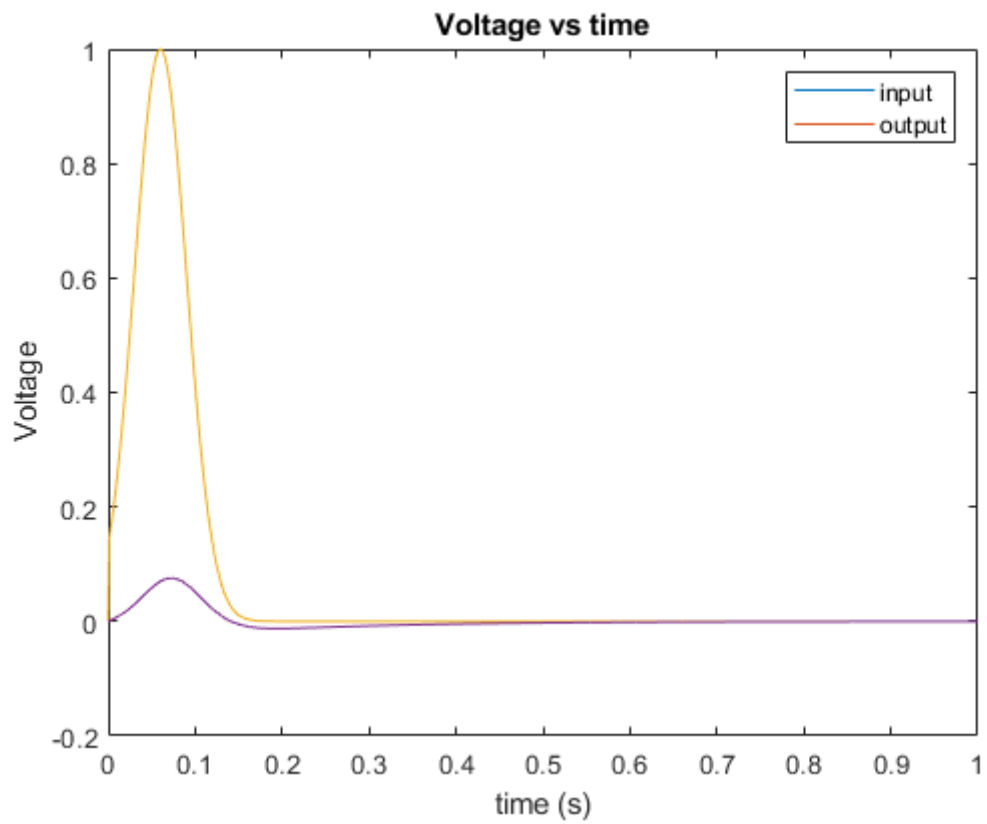

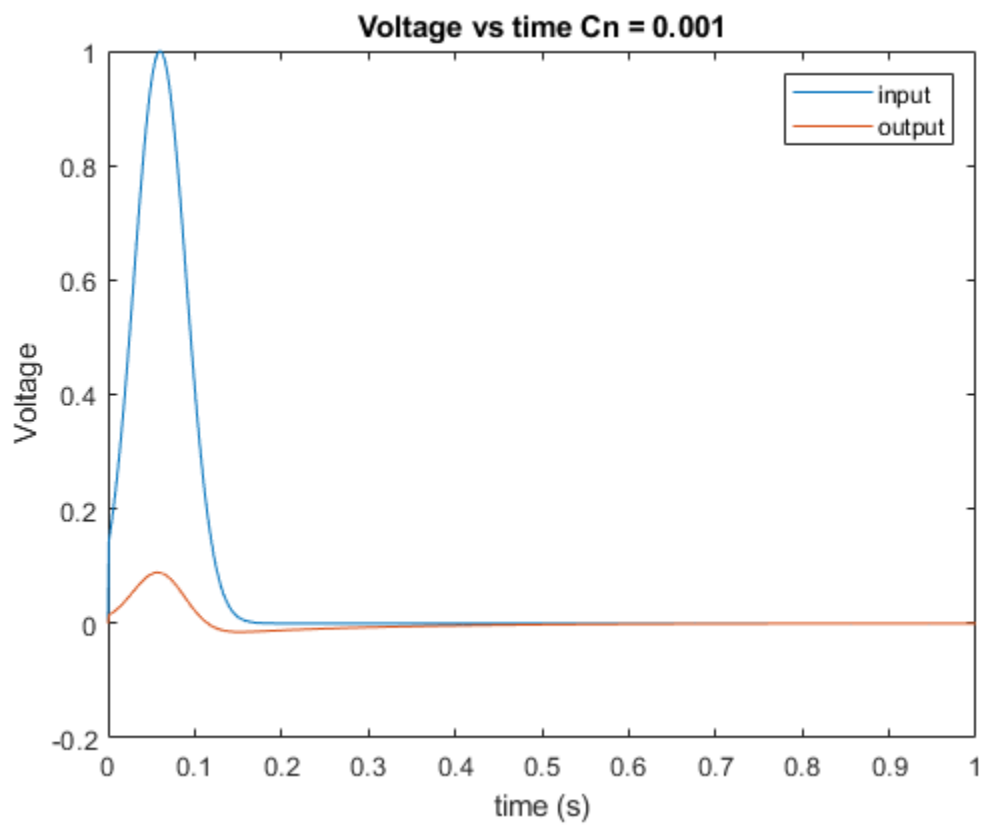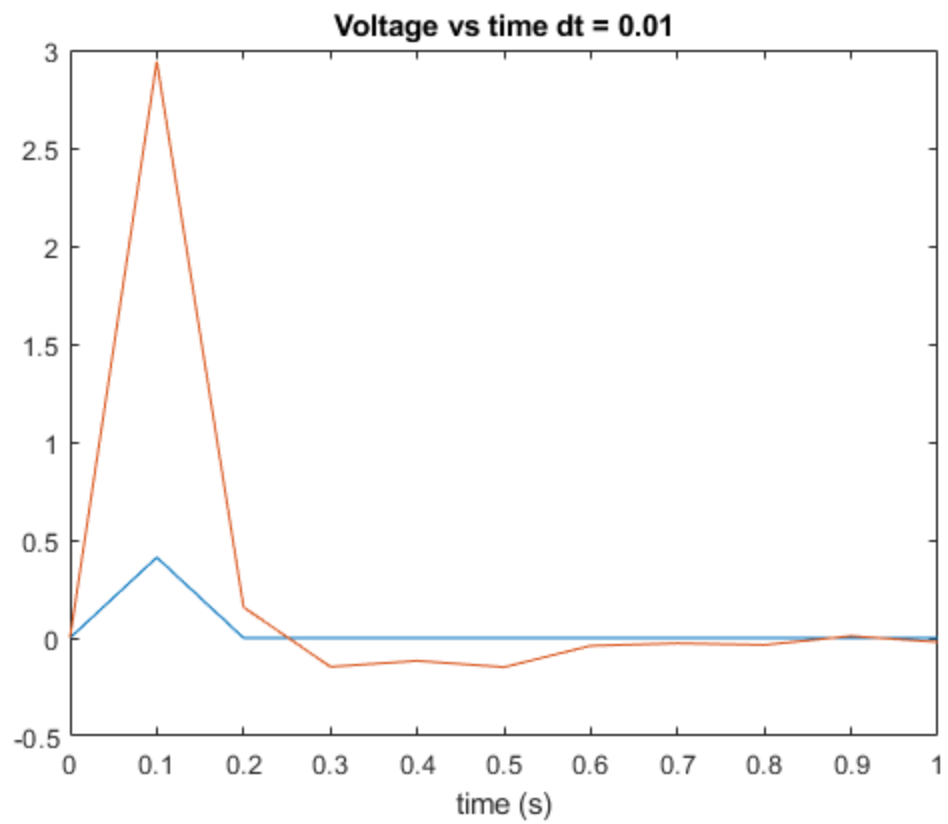

These results show that as the step is increased, the results of the simulation can become very erratic / inaccurate. This is because the accuracy of the finite difference approximation is inversely proportional to the step size.

```
figure(10)
plot(0:dt:1,Vi)
hold on
plot(0:dt:1,Vo_2)
title('Voltage vs time Cn = 0.001')
xlabel('time (s)')
ylabel('Voltage')
legend('input','output')
```

```
figure(11)
plot(0:dt2:1,ViLargeStep)
hold on
plot(0:dt2:1,VoLargeStep)
title('Voltage vs time dt = 0.01')
xlabel('time (s)')
```